

CSM CS61C Note #5: Finite State Machines (FSM), RISC-V Single-Cycle Datapath

Anthony Han

1 Boolean Algebra

Notation

- Plus “+” for OR - “logical sum.”
- Product “.” for AND - “logical product.”
- Hat “¬” for NOT - complement.

Truth Table for Combinational Logic

Exhaustive list of the output value generated for each combination of inputs. For a logic function with 3 inputs, we can do a truth table:

<i>a</i>	<i>b</i>	<i>c</i>	<i>y</i>
0	0	0	$F(0,0,0)$
0	0	1	$F(0,0,1)$
0	1	0	$F(0,1,0)$
0	1	1	$F(0,1,1)$
1	0	0	$F(1,0,0)$
1	0	1	$F(1,0,1)$
1	1	0	$F(1,1,0)$
1	1	1	$F(1,1,1)$

Given a truth table, we can derive its logic function as

$$F = \sum_{F(x_1, \dots, x_n) = 1} \prod_{i=1}^n \phi(x_i)$$


$$\text{where } \phi(x_i) = \begin{cases} x_i & x_i == 1 \\ (\sim x_i) & x_i == 0 \end{cases}.$$

Laws of Boolean Algebra

$X\bar{X} = 0$	$X + \bar{X} = 1$	Complementarity
$X0 = 0$	$X + 1 = 1$	Laws of 0's and 1's
$X1 = X$	$X + 0 = X$	Identities
$XX = X$	$X + X = X$	Idempotent Laws
$XY = YX$	$X + Y = Y + X$	Commutativity
$(XY)Z = X(YZ)$	$(X + Y) + Z = X + (Y + Z)$	Associativity
$X(Y + Z) = XY + XZ$	$X + YZ = (X + Y)(X + Z)$	Distribution
$XY + X = X$	$(X + Y)X = X$	Uniting Theorem
$\bar{X}Y + X = X + Y$	$(\bar{X} + Y)X = XY$	Uniting Theorem v2
$(\bar{X}Y) = \bar{X} + \bar{Y}$	$(\bar{X} + \bar{Y}) = \overline{XY}$	DeMorgan's Law

Boolean Algebra Simplifies Circuits

 Given this circuit that implements $y = ab + a + c$, we could do gate minimization.



Using some boolean algebra, we get

$$\begin{aligned}
 y &= ab + a + c \\
 &= a(b + 1) + c \\
 &= a(1) + c \\
 &= a + c.
 \end{aligned}$$


And we can simplify the gates.




2 Finite State Machines (FSM)

Finite State Machines (FSM) Intro

 - A convenient way to conceptualize computation over time.
- Start at a state and given an input, follow some edge to another (or the same) state.
- The function can be represented with a “state transition diagram.”
- With combinational logic and registers, any FSM can be implemented in hardware.



 FSM Example: Detecting Three Consecutive 1's in the Input**3 RISC-V Single-Cycle Datapath****“State” Required by RV32I ISA**


If we treat a RISC-V processor as a FSM, then each instruction reads and updates this state during execution:

- **Registers** (x_0, \dots, x_{31})
 - **Register file (or *regfile*)** Reg holds 32 registers \times 32 bits/register: $\text{Reg}[0], \dots, \text{Reg}[31]$.
 - **First register read** specified by *rs1* field in instruction.
 - **Second register read** specified by *rs2* field in instruction.
 - **Write register (destination)** specified by *rd* field in instruction.
 - x_0 is always 0 (**writes to $\text{Reg}[0]$ are ignored**).
- **Program Counter (PC)**
 - Holds address of current instruction.
- **Memory (MEM)**
 - Holds both instructions & data, in one 32b byte-addressed memory space.
 - We'll use **separate memories for instructions (IMEM) and data (DMEM)**.
Later, these will be replaced with instruction and data caches.
 - Instructions are fetched from instruction memory (assume IMEM read-only).
 - Load/store instructions access data memory.


One-Instruction-Per-Cycle RISC-V Machine

First let's see a single cycle model: on every tick of the clock, the computer executes one instruction.

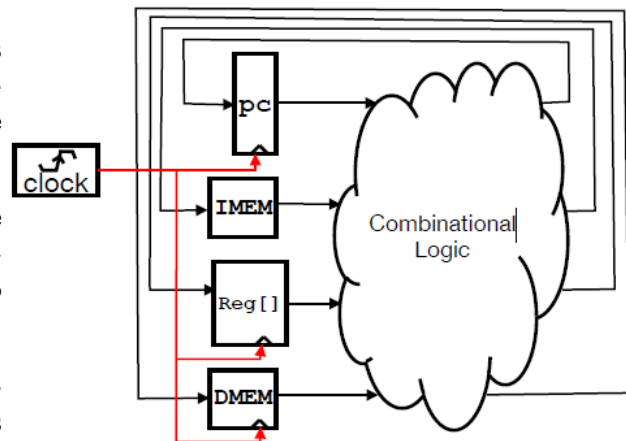
1. **Current state outputs drive the inputs to the combinational logic, whose outputs settle at the values of the state before the next clock edge.**
2. **At the rising clock edge, all the state elements are updated with the combinational logic outputs, and execution moves to the next clock cycle.**
3. **Separate instruction/data memory:** For simplification, memory is **asynchronous read** (not clocked), but **synchronous write** (is clocked).



Basic Phases of Instruction Execution

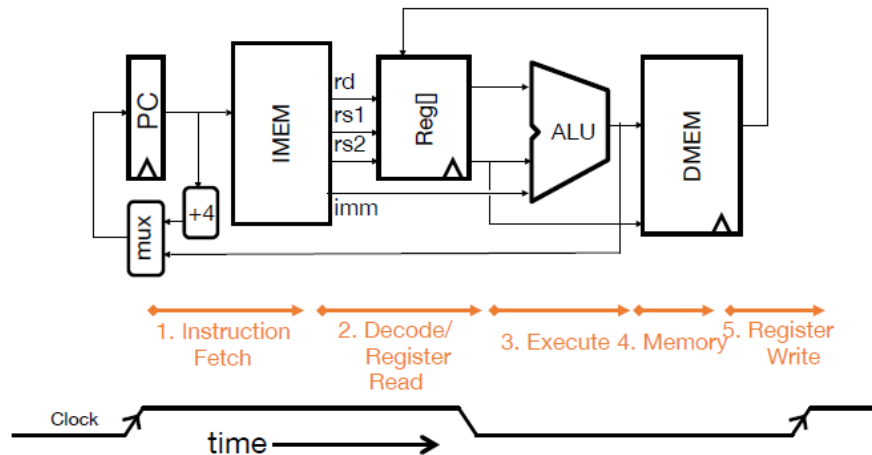

Single-Cycle RISC-V RV32I Datapath

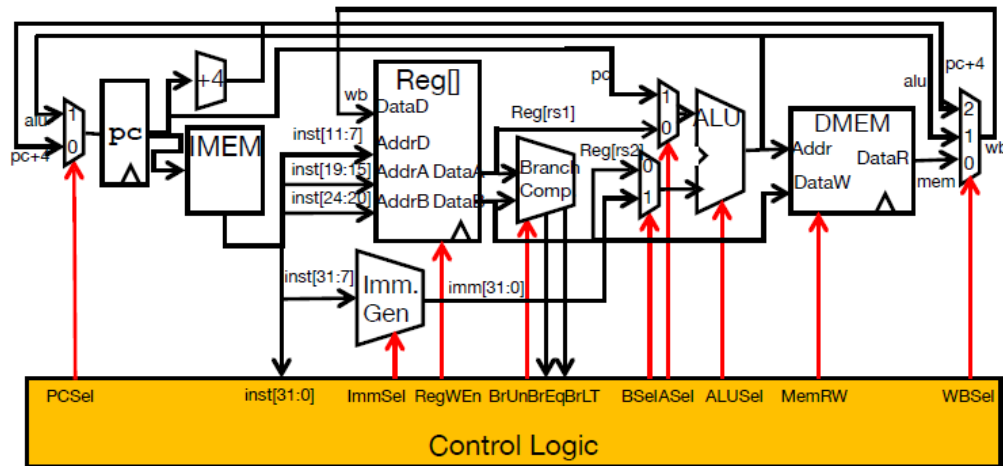

- **Universal datapath** - capable of executing all RISC-V instructions in one cycle each.
- 5 phases of execution:
 - **IF** - instruction fetch;
 - **ID** - instruction decode;
 - **EX** - execute;
 - **MEM** - memory access;
 - **WB** - write back.
- Not all units and phases are used in every instruction.
- Controller specifies how to execute instructions.

RISC-V Single-Cycle Control

A simple way to do the control logic is to implement a **truth table**:

Inst[31:0]	BrEq	BrLT	PCSel	ImmSel	BrUn	ASel	BSel	ALUSel	MemRW	RegWEn	WBSel
add	*	*	+4	*	*	Reg	Reg	Add	Read	1	ALU
sub	*	*	+4	*	*	Reg	Reg	Sub	Read	1	ALU
(R-R Op)	*	*	+4	*	*	Reg	Reg	(Op)	Read	1	ALU
addi	*	*	+4	I	*	Reg	Imm	Add	Read	1	ALU
lw	*	*	+4	I	*	Reg	Imm	Add	Read	1	Mem
sw	*	*	+4	S	*	Reg	Imm	Add	Write	0	*
beq	0	*	+4	B	*	PC	Imm	Add	Read	0	*
beq	1	*	ALU	B	*	PC	Imm	Add	Read	0	*
bne	0	*	ALU	B	*	PC	Imm	Add	Read	0	*
bne	1	*	+4	B	*	PC	Imm	Add	Read	0	*
blt	*	1	ALU	B	0	PC	Imm	Add	Read	0	*
bltu	*	1	ALU	B	1	PC	Imm	Add	Read	0	*
jalr	*	*	ALU	I	*	Reg	Imm	Add	Read	1	PC+4
jal	*	*	ALU	J	*	PC	Imm	Add	Read	1	PC+4
auipc	*	*	+4	U	*	PC	Imm	Add	Read	1	ALU

inst[31:2]				inst[14:12]				inst[6:2]			
imm[31:12]			rd	0110111	LUI						
imm[31:12]			rd	0010111	AUIPC						
imm[20:10] 19:12			rd	1101111	JAL						
imm[11:9]		rs1	rd	1100111	JALR						
imm[29:15]	rs2	rs1	000	1100111	BNE						
imm[29:15]	rs2	rs1	001	1100111	BREQ						
imm[29:15]	rs2	rs1	100	1100111	BLT						
imm[29:15]	rs2	rs1	101	1100111	BGE						
imm[29:15]	rs2	rs1	110	1100111	BLTU						
imm[29:15]	rs2	rs1	111	1100111	BGEU						
imm[11:9]		rs1	000	0000111	LB						
imm[11:9]		rs1	001	0000111	LBH						
imm[11:9]		rs1	010	0000111	LW						
imm[11:9]		rs1	100	0000111	LBU						
imm[11:9]		rs1	101	0000111	LHU						
imm[11:5]	rs2	rs1	000	0100111	SB						
imm[11:5]	rs2	rs1	001	0100111	SH						
imm[11:5]	rs2	rs1	010	0100111	SW						
imm[11:9]		rs1	000	0010111	ADDI						
imm[11:9]		rs1	010	0010111	SLTI						
imm[11:9]		rs1	011	0010111	SLTIU						
imm[11:9]		rs1	100	0010111	XORI						
imm[11:9]		rs1	110	0010111	ORI						
imm[11:9]		rs1	111	0010111	ANDI						

- ROM - Read-Only Memory

-
- Inst[10:0] → 11 → Address Decoder
- | |
|-----------------------------|
| Control Word for add |
| Control Word for sub |
| Control Word for or |
| . |
| . |
| . |
| . |
| . |
- Controller output (PCSel, ImmSel, ...)

-
- 11-bit address (inputs)
- Inst[30,14:12,6:2] BrEq BrLT
- 9
- Combinational Logic Function(s)
- 3 PCSel ImmSel[2:0]
- BrUn ASel BSel
- 4 ALUSel[3:0]
- MemRW RegWEn WBSel[1:0]
- 2
- 15 data bits (outputs)